
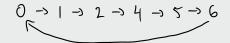
<u>Problem statement</u>: Implement the sequential circuit needed for the following sequence (using Tf/f)




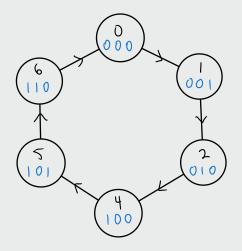


Q(t)	Q(t + 1)	Т
0	0	0
0	1	1
1	0	1
1	1	0
	(d) T	

T flip flop Excitation table

_	Q(t)			Q(t+1)						
	Α	B	\subset	A	В		Ta	TB	T_{c}	
0	0	0	0	0	0	1	0	0	1	
1	0	0	1	0	1	0	0	l	I	
2	ð	1	0	(0	0	1	١	0	
4	1	0	0		0	1	v	0	1	
5	1	O	1		1	0	0	1)	
6	1	l	0	0	0	0)	١	0	

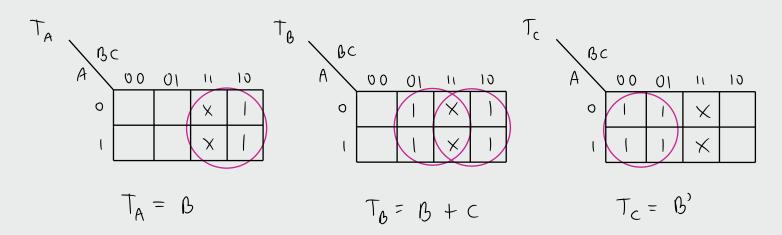

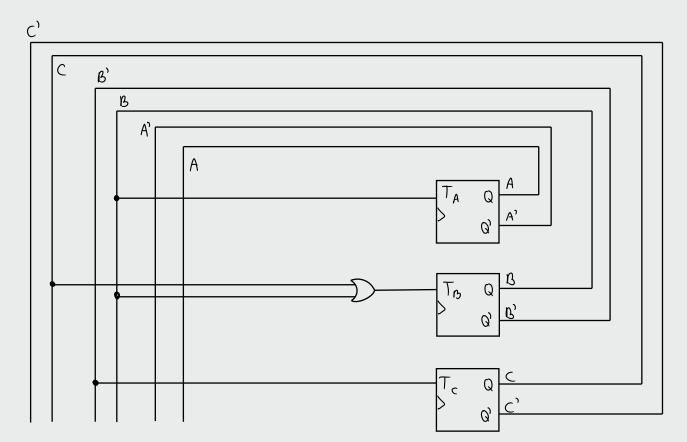Note: Failure to simplify to the simplest boolean expression can lead to incorrectly determining which states the invalid states transition to, potentially leading to an incorrect conclusion as to whether the circuit is self-correcting or not.



$$\begin{array}{c|c}
T & Q(t+1) \\
\hline
0 & Q(t) \\
\hline
1 & Q'(t)
\end{array}$$

T flip flop characteristic table


Unused State 011

$$\begin{array}{c|cccc}
\hline
A & B & C \\
\hline
O & I & I \\
\hline
I & B & E \\
I & B & E \\
\hline
I &$$

Unuxed State 111

A B C
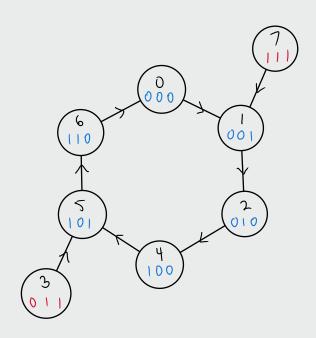
$$T_A = B = 1 \implies toggle$$
 $T_B = B + C = 1 + 1$
 $T_C = B$
 $T_C = B$
 $T_C = B$
 $T_C = B$
 $T_C = B$



Since the invalid states transition to valid states

(011 -> 100 and 111 -> 001),

then this circuit is self correcting