

# Memory

1 cell = 1 bit

8 cells = 8 bits = 1 byte

4 bytes = 1 word (in MIPS)

Read: uses MUX

Write: In order to get to a specific location: uses decoders

Memory is built from small components to bigger components

To access a specific memory location: we access the bigger structures first (big  $\rightarrow$  small access strategy)

## Addressing

\* MIPS uses byte Addressing

To represent the number of addressable units in a system:

$2^k \times m$  where  $k$  is the Address size,  $m$  = word size

$2^k$  distinct addresses  $\rightarrow 2^k$  distinct words

## Array of RAM chips

We can increase memory chips or increase the size of a word

If we have the RAM config  $1K \times 8 = 2^{10} \times 8$  ( $1K = 2^{10} = 1024 \rightarrow$  has 1024 words, each word being 8 bits)

Say we want to increase our memory capacity by 10  $\rightarrow$  we want to have 10240 words

We'll put 10 chips together  $\rightarrow C_0$  to  $C_9$

- Say we then want to access word 3079, then we need to have a method for how we can access the correct memory location.

- Since we have 1024-word chips, then we consider that if we want to find word 1023, it will be on the first chip,  $C_0$ , and word 1024 on  $C_1$


$\hookrightarrow 3079 = 1024 \times 3 + 7 \Rightarrow$  our target word is on chip 3 with a word offset of 7

$$3079 = 3 \times 1024 + 7 = \begin{matrix} 2 \times 1024 & + & 1024 & + & 7 \\ \downarrow & & \downarrow & & \downarrow \\ 2^{11} & + & 2^{10} & + & 111 \end{matrix}$$

Absolute Address: 

1	1	0	0	0	0	0	0	1	1	1	
11	10	9	8	7	6	5	4	3	2	1	0

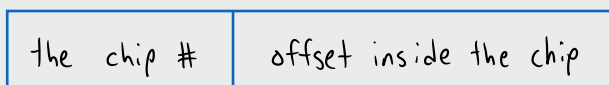
If we have 32-bit Addresses, then we'll have to pad the absolute address with a bunch of zeros  
 The absolute Address is partitioned (from right to left) into fields



The size of the offset = size of the chip's address

↳ in our case, the originally stated memory config was  $1K \times 8 \rightarrow$  the address is 10 bits (since  $1K = 2^{10}$ )

32 bit Address:

 

We'll implement a decoder to act as our chip selector. Since we have 10 chips, we need to implement a decoder that accepts a 4-bit input to accommodate all possible chip selections 0-9

\* CS = Chip Select

