

BCD (digital display)

Following the example covered in class, get the simplified of a

A digital clock face is a grid of lights:




\Rightarrow A clock face with all lights turned off




\Rightarrow A clock face representing the number 7 with 3 lights turned on

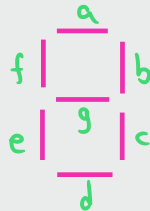So we can assign a variable to each light to control which turns on to represent any number 0-9 \Rightarrow



I_3	I_2	I_1	I_0	Decimal # that we want to represent	a b c d e f g
0	0	0	0	0	1 1 1 1 1 1 0
0	0	0	1	1	0 1 1 0 0 0 0
0	0	1	0	2	1 1 0 1 1 0 1
0	0	1	1	3	1 1 1 1 0 0 1
0	1	0	0	4	0 1 1 0 0 1 1
0	1	0	1	5	1 0 1 1 0 1 1
0	1	1	0	6	1 0 1 1 1 1 1
0	1	1	1	7	1 1 1 0 0 0 0
1	0	0	0	8	1 1 1 1 1 1 1
1	0	0	1	9	1 1 1 0 0 1 1
1	0	1	0	X	x x x x x x x
1	0	1	1	X	x x x x x x x
1	1	0	0	X	x x x x x x x
1	1	0	1	X	x x x x x x x
1	1	1	0	X	x x x x x x x
1	1	1	1	X	x x x x x x x

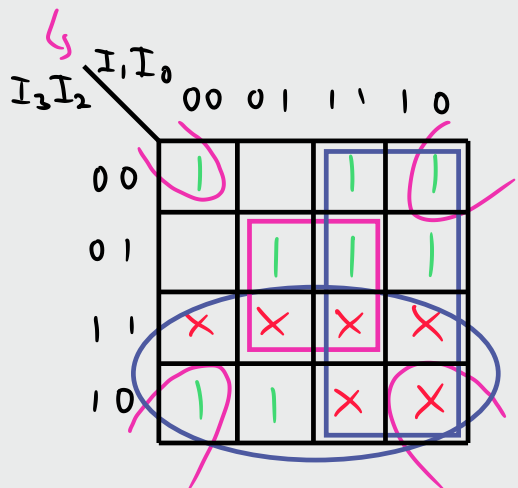Since we want the boolean expression that outputs g, we select the entire column of a and feed it to a K-map.



$$I_2'I_0 + I_2I_0 + I_3 + I_1$$

\hookrightarrow Simplified expression of a

we don't use these

Don't Cares